

Carleton University
Department of Systems and Computer Engineering
SYSC 3006 (Computer Organization) Fall 2020
Lab / Assignment 4– Answers file

Student Name: Youssef Ibrahim

ID#: 101103080

Part 1 – [2.4-mark/5]

1-1

- a) [0.50-mark] Fill in the Part 1 Instruction Encoding Table for the following instructions.

OPR	Instruction	Encoding (hex)
NOT	$R5 \leftarrow \text{NOT } R4$	0x07504000
SUB	$R7 \leftarrow R6 - R5$	0x02765000
NOP	NOP	0x00000000
MOV	$R0 \leftarrow R7$	0x03007000

c) [0.50-mark] Complete the FSM Decode ROM Tables (this table is same for Part 1 and 2 of this lab).

Instruction	Address (hex)	Contents (hex)
NOP	00	00
ADD	01	04
SUB	02	04
MOV	03	05
AND	04	04
OR	05	04
XOR	06	04
NOT	07	05

NOTE: In the supplied circuit, the Control FSM outputs the RegSEL and RegLD signals with the behaviour expected by the Registers RAM. The FSM Output ROM does not use RegR and RegW signals as done in Lab-3 and in class; the RegSEL and RegLD signals (with Logisim RAM signaling behaviour) are used instead.

Do not change any of the values that have been pre-entered into the table, except for the empty cases in the hexadecimal encodings (in Part 1 FSM Output ROM Table). The first 3 states are there only as placeholders in Part 1 and have been designed to have no undesirable effects on the circuit. This allows you to always start the FSM in state 0.

The resulting FSM Output ROM and FSM Decode ROM values should work for any of the instructions discussed in class that use the ALU (i.e. NOP, ADD, SUB, MOV, AND, OR, XOR and NOT).

- d) [0.50-mark] Save your circuit as Lab-4_Part1.circ. and submit it with your assignment for verification and to get the marks for this section.
- e) [0.40-mark] Same as you did in lab 3, execute the instructions in the table above in the given sequence with all registers initially containing 0x0. Log the execution of the sequence on your implementation to validate the execution of the required instructions and show the results here. (The simulation log should include: Current State, IR, PC, registers, and Next State. Set the log radix to hex).

Logisim: Log main of Lab4Part1

File Edit Project Simulate Window Help

Selection Table File

Current State	Next State	Instruction Register	RAM(1060,270)[0]	RAM(1060,270)[5]	RAM(1060,270)[6]	RAM(1060,270)[7]	RAM(1060,270)[15]
00	01	07504000	00000000	00000000	00000000	00000000	00000000
01	02	07504000	00000000	00000000	00000000	00000000	00000000
02	03	07504000	00000000	00000000	00000000	00000000	00000000
03	05	07504000	00000000	00000000	00000000	00000000	00000000
05	06	07504000	00000000	00000000	00000000	00000000	00000000
06	00	07504000	00000000	00000000	00000000	00000000	00000000
06	00	07504000	00000000	ffffff	00000000	00000000	00000000
00	01	02765000	00000000	ffffff	00000000	00000000	00000000
01	02	02765000	00000000	ffffff	00000000	00000000	00000000
02	03	02765000	00000000	ffffff	00000000	00000000	00000000
03	04	02765000	00000000	ffffff	00000000	00000000	00000000
04	05	02765000	00000000	ffffff	00000000	00000000	00000000
05	06	02765000	00000000	ffffff	00000000	00000000	00000000
06	00	02765000	00000000	ffffff	00000000	00000000	00000000
06	00	02765000	00000000	ffffff	00000000	00000001	00000000
00	01	00000000	00000000	ffffff	00000000	00000001	00000000
01	02	00000000	00000000	ffffff	00000000	00000001	00000000
02	03	00000000	00000000	ffffff	00000000	00000001	00000000
03	00	00000000	00000000	ffffff	00000000	00000001	00000000
00	01	03007000	00000000	ffffff	00000000	00000001	00000000
01	02	03007000	00000000	ffffff	00000000	00000001	00000000
02	03	03007000	00000000	ffffff	00000000	00000001	00000000
03	05	03007000	00000000	ffffff	00000000	00000001	00000000
05	06	03007000	00000000	ffffff	00000000	00000001	00000000
06	00	03007000	00000000	ffffff	00000000	00000001	00000000
06	00	03007000	00000001	ffffff	00000000	00000001	00000000

Part 2 – [total of 2.6-mark/5]

2.1 - Tables

a) [0.50-mark] Complete the Part 2 FSM Output ROM Table.

	State Hex encoding																																	
	Unused (0)	31																																
	IRCE	30																																
	PCOE	29																																
	C1OE	28																																
	AADD	27																																
	MARCE	26																																
	MAROE	25																																
	MDRCE	24																																
	MDROE	23																																
	MDRget	22																																
	MDRput	21																																
	IBRead	20																																
	IBWrite	19																																
	AOP	18																																
	ANOP	17																																
	DR	16																																
	SXR	15																																
	SYR	14																																
	RegSEL	13																																
	RegID	12																																
	T1CE	11																																
	T1OE	10																																
	T2CE	9																																
	T2OE	8																																
	Q7+	7																																
	Q6+	6																																
	Q5+	5																																
	Q4+	4																																
	Q3+	3																																
	Q2+	2																																
	Q1+	1																																
	Q0+	0																																
	Hex Encoding																																	
F0 0	0	0	0	1	0	0	1	0	0	0	0	0	0	0	1	0	0	0	1	1	1	0	0	0	0	0	0	0	0	0	1	24023801		
F1 1	0	0	0	1	1	0	1	1	0	0	0	1	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	0	0	1	0	1B100602		
F2 2	0	1	0	0	0	0	0	0	1	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	40C20003		
Decod e 3	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	1	0	0	0	0	1	0	0	0	0	0	1	1	1	20022107	
E0 4	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	0	1	1	1	0	0	0	0	0	0	0	1	0	1	0002B805		
E1 5	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	1	1	1	0	1	1	0	0	0	0	0	1	1	0	00047606		
E2 6	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0	1	0	0	0	0	1	0	0	0	0	0	0	0	00032100		
Dead 7	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	0000 0007		


b) [0.40-mark] Complete the Part 2 Main Memory Instructions Table for the following instructions.

Instruction	Address (hex)	Contents (hex)
$R10 \leftarrow R1 \text{ OR } R2$	00	0x05A12000
$R11 \leftarrow R2 - R10$	01	0x02B2A000
$R12 \leftarrow \text{NOT } (R11)$	02	0x07C0B000
$R13 \leftarrow R0 + R12$	03	0x01D0C000


2.2 - Circuit wiring

Save a copy of your part 1 (Save as) and name it "Lab4-Part-2.circ". Then extend your Processor solution to Part 1 to read and execute instructions from Main Memory. You will not need to modify the circuit beyond the description of modifications given above.

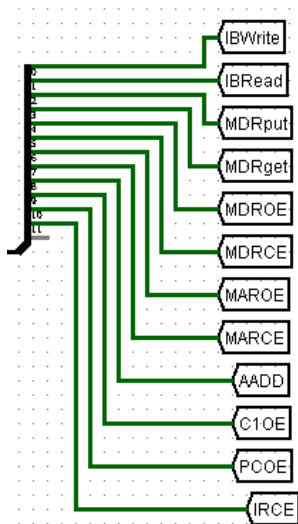
a) [0.30-mark] Show below a screenshot of the new control FMS outputs that you added in the Logisim circuits, and a short description about each output.





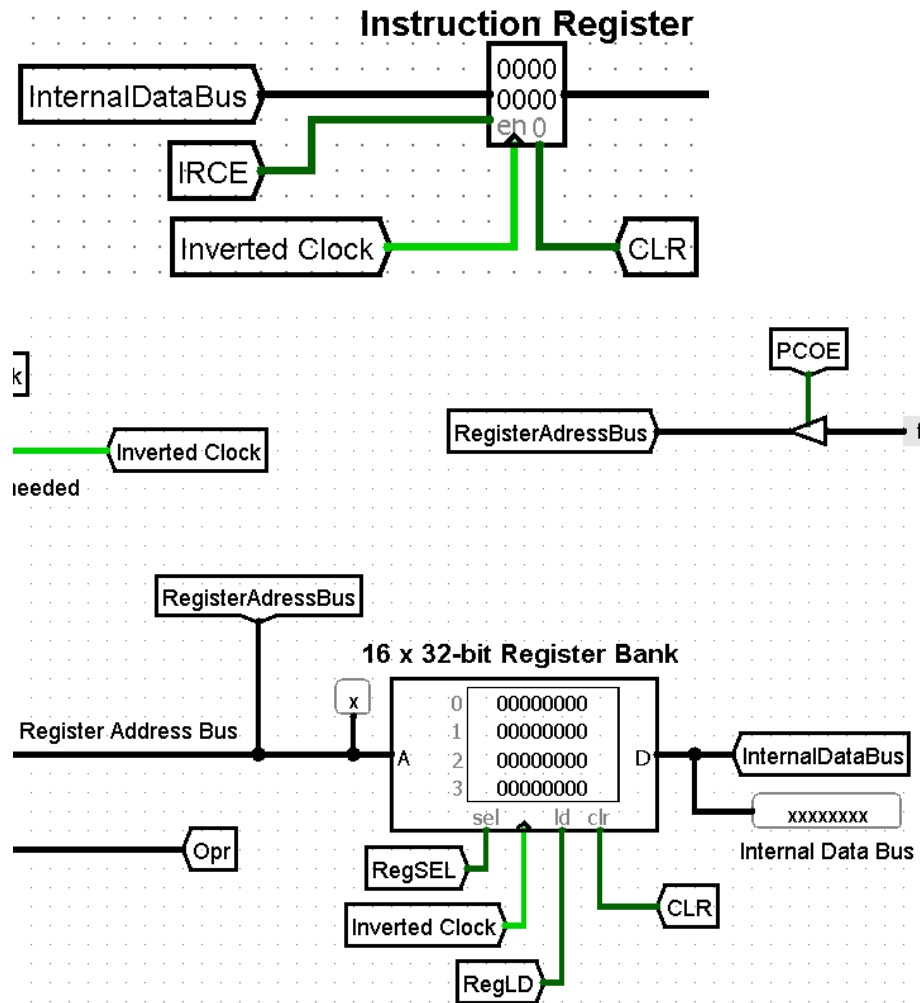- b) [0.40-mark] Show here a screenshot of the new hardware components that you added in the Logisim circuits. Include a short description about each component function.



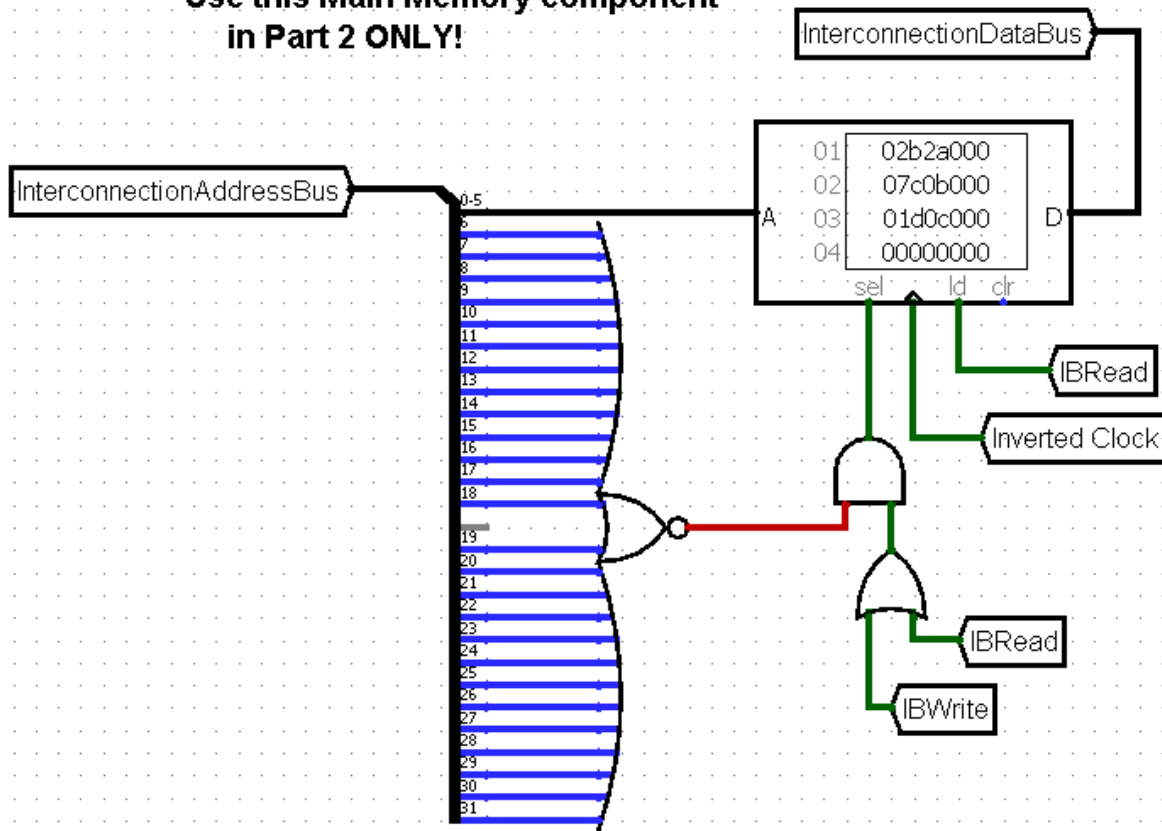**Use this Main Memory component
in Part 2 ONLY!**



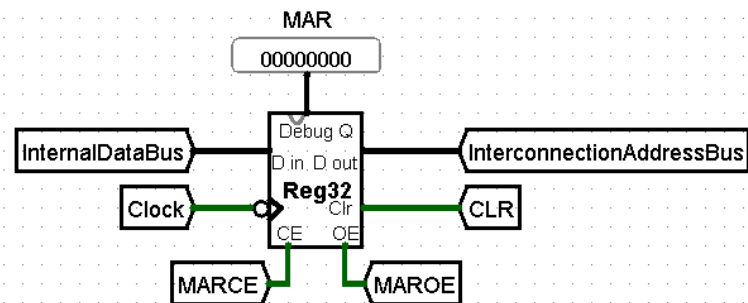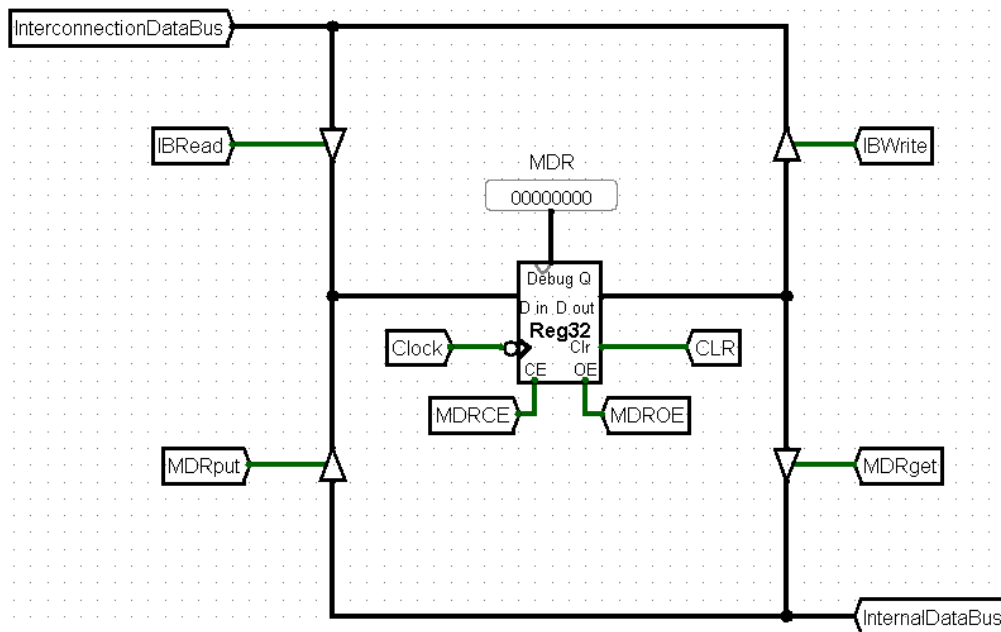

- c) [0.30-mark] Include a copy of your Lab4-Part-2.circ circuit with your submission. We must verify your circuit functionality in order to assign you marks for this part (c)

2.3 Execution test

- a) [0.40-mark] The Part 2 Main Memory Instructions Table in 2.1 –b) contain same instruction sequence from your lab 3-part 2, but here they are encoded over 32-bit word width. Clear the 16 internal register bloc and the Main memory to 0x0. Then as you did in lab 3, initiate R0 to 0x00000001, R1 to 0x1000000F and R2 to 0xF0000000. Then insert the instructions from the Table in 2.1 –b) above into the Main Memory starting at address 0 and up (one instruction per address word as indicated in the table) in the given sequence. Now, execute all the instructions (repeat fetch-decode-execute cycle till all instruction are fully executed). To execute all instruction just poke the Toggle Switch to advance the FSM through the operation till all instructions are fully executed (while observing their execution). Make sure you PC (R15), holds the address of the first instruction to be fetched, then observe it increments... to fetch the next... Same as you did in part 1, log the execution of the sequence on your implementation to validate the execution of the required instructions and show the results here.

Logisim: Log main of Lab4-Part2

File Edit Project Simulate Window Help

Selection Table File

Current State	Next State	Instruction Register	RAM(1060,270)[0]	RAM(1060,270)[1]	RAM(1060,270)[2]	RAM(1060,270)[10]	RAM(1060,270)[11]	RAM(1060,270)[12]	RAM(1060,270)[13]	RAM(1060,270)[15]
00	01	00000000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000000
01	02	00000000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000000
02	03	00000000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000000
02	03	05a12000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000000
03	04	05a12000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000000
03	04	05a12000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000001
04	05	05a12000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000001
05	06	05a12000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000001
06	00	05a12000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000001
06	00	05a12000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000001
00	01	05a12000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000001
01	02	05a12000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000001
02	03	05a12000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000001
02	03	02b2a000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000001
03	04	02b2a000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000001
03	04	02b2a000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000002
04	05	02b2a000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000002
05	06	02b2a000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000002
06	00	02b2a000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000002
06	00	02b2a000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000002
00	01	02b2a000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000002
01	02	02b2a000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000002
02	03	02b2a000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000002
02	03	07c0b000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000002
03	05	07c0b000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000002
03	05	07c0b000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000003
05	06	07c0b000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000003
06	00	07c0b000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000003
06	00	07c0b000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000003
00	01	07c0b000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000003
01	02	07c0b000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000003
02	03	07c0b000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000003
02	03	01d0c000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000003
03	04	01d0c000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000003
03	04	01d0c000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000004
04	05	01d0c000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000004
05	06	01d0c000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000004
06	00	01d0c000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000004
06	00	01d0c000	00000001	1000000f	f0000000	00000000	00000000	00000000	00000000	00000004

- b) [0.30-mark] Compare the concept used here to your lab 3-part 2, briefly describe here what is the advantage of the concept here over lab3-part 2?

In this lab, the instructions were loaded into the IR automatically, however in lab 3-part 2, instructions were needed to be put in the IR manually. Hence, the concept used in this lab is more efficient as it saves time and automates the process.

Submission deadline

Must be submitted on cuLearn, locate (Assignment 4 submission) and follow instructions. Submission exact deadline (date and time) is displayed clearly within the Assignment 4 submission on cuLearn.

Note: If you have any question please contact your respective group TA (see TA / group information posted on cuLearn) or use Discord class server.

Good Luck